

Coffee machine hardware modifications

This document explains how you can easily hack a cheap filter coffee maker and interface it with the Intel Edison breakout board.


Material

- Intel Edison Breakout board ([Here](#))
- Breadboard ([Here](#))
- 5V 10A Relay module (optocoupled) ([Here](#))
- 2 Transistor BC547 ([Here](#))
- 2 Diodes 1N4148 ([Here](#))
- 2 LEDs (facultative) ([Here](#))
- Wires, headers, soldering iron

Step 1 : Prepare the Edison board


The Intel Edison Breakout board exposes Edison GPIOs to the bottom of the board. Besides, it comes without headers pins and you need to add them by yourself.

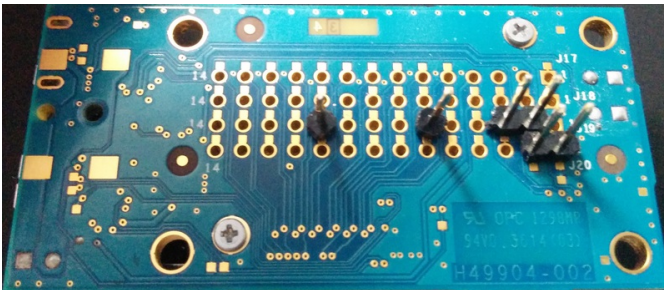We will use **J20-2** (3.3V) **J19-3** (GND) **J19-6** (GPIO 48 - LED) **J19-10** (GPIO 40 - Relay).



As next step, you'll see that the 1.8V logical levels from the Edison are too small to light an LED or to pilot the relay module. Without level shifting, the Edison has 1.8V voltage levels.

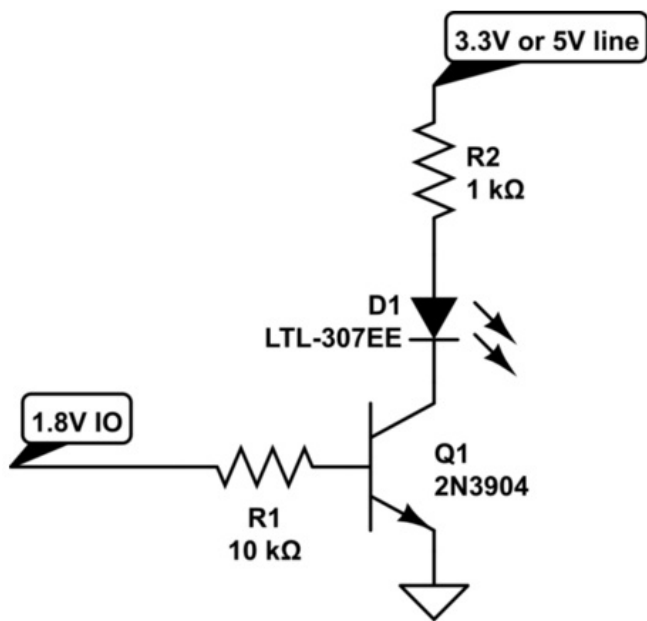To solve this problem, you may use a transistor. That what we will do in step 3.
The schematic looks as below:



Step 2 : Disassemble the machine power block

Unscrew the coffee make power block cover. Usually, it is at the bottom.

It should look like the next picture :




Step 3 : Wire the machine to the Relay

Cut the phase wire, which is the brown one in the Step 2 picture.

Then, connect each end to the relay module, as in the next picture. The relay module will act as a switch that you can control with the Edison board.

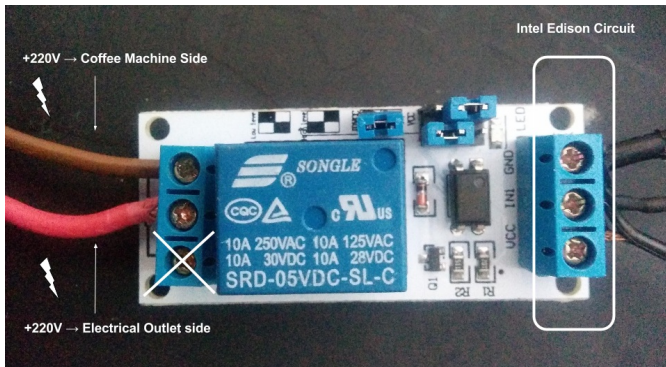
Note that you may need to extend the wire length to place the relay module with more convenience.



Step 4 : Wire the circuit

Finally, wire the control circuit, to interface the Intel Edison GPIO with the relay module on the breadboard, like in the following image.

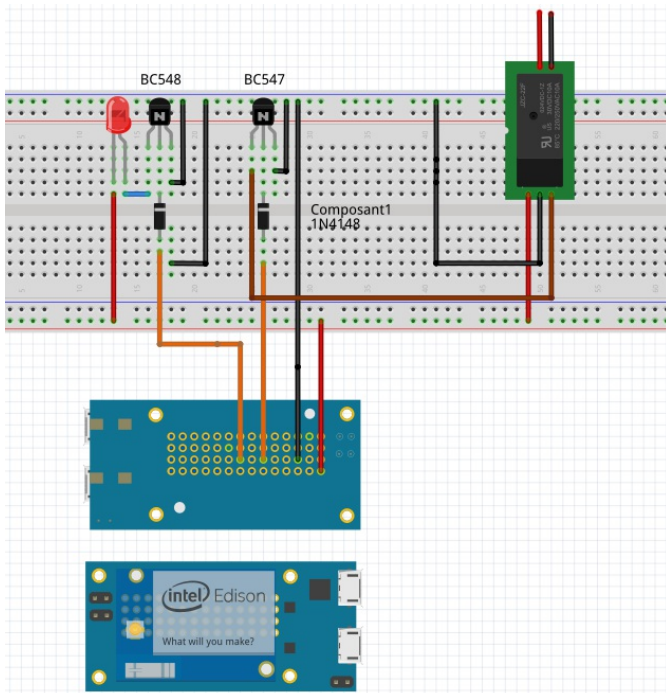Your Intel Edison board can now control the coffee maker



Since you ensure everything works, next step is building a tiny case for the Intel EDISON and the circuit following this [tutorial](#)